

Multiplier:

a_0, b_0

```
and_gate1: AND_gate port map(a => A(0), b => B(0), output => AB0(0));
and_gate2: AND_gate port map(a => A(1), b => B(0), output => AB0(1));
and_gate3: AND_gate port map(a => A(2), b => B(0), output => AB0(2));
and_gate4: AND_gate port map(a => A(3), b => B(0), output => AB0(3));
```

a_1, b_1



```
and_gate5: AND_gate port map(a => A(0), b => B(1), output => AB1(0));
and_gate6: AND_gate port map(a => A(1), b => B(1), output => AB1(1));
and_gate7: AND_gate port map(a => A(2), b => B(1), output => AB1(2));
and_gate8: AND_gate port map(a => A(3), b => B(1), output => AB1(3));
```

```
and_gate9: AND_gate port map(a => A(0), b => B(2), output => AB2(0));
and_gate10: AND_gate port map(a => A(1), b => B(2), output => AB2(1));
and_gate11: AND_gate port map(a => A(2), b => B(2), output => AB2(2));
and_gate12: AND_gate port map(a => A(3), b => B(2), output => AB2(3));
```

a_2, a_3

```
and_gate13: AND_gate port map(a => A(0), b => B(3), output => AB3(0));
and_gate14: AND_gate port map(a => A(1), b => B(3), output => AB3(1));
and_gate15: AND_gate port map(a => A(2), b => B(3), output => AB3(2));
and_gate16: AND_gate port map(a => A(3), b => B(3), output => AB3(3));
```

```
FA1: full_adder port map( a => AB0(2), b => AB1(1), Cin => C1(0), Cout => C1(1), sum => P1(1));
FA2: full_adder port map( a => AB0(3), b => AB1(2), Cin => C1(1), Cout => C1(2), sum => P1(2));
FA3: full_adder port map( a => P1(2), b => AB2(1), Cin => C2(0), Cout => C2(1), sum => P2(1));
FA4: full_adder port map( a => P1(3), b => AB2(2), Cin => C2(1), Cout => C2(2), sum => P2(2));
FA5: full_adder port map( a => C1(3), b => AB2(3), Cin => C2(2), Cout => C2(3), sum => P2(3));
FA6: full_adder port map( a => P2(2), b => AB3(1), Cin => C3(0), Cout => C3(1), sum => P3(1));
FA7: full_adder port map( a => P2(3), b => AB3(2), Cin => C3(1), Cout => C3(2), sum => P3(2));
FA8: full_adder port map( a => C2(3), b => AB3(3), Cin => C3(2), Cout => C3(3), sum => P3(3));
HA1: half_adder port map( a => AB0(1), b => AB1(0), cout => C1(0), sum => P1(0));
HA2: half_adder port map( a => AB1(3), b => C1(2), cout => C1(3), sum => P1(3));
HA3: half_adder port map( a => P1(1), b => AB2(0), cout => C2(0), sum => P2(0));
HA4: half_adder port map( a => P2(1), b => AB3(0), cout => C3(0), sum => P3(0));
```

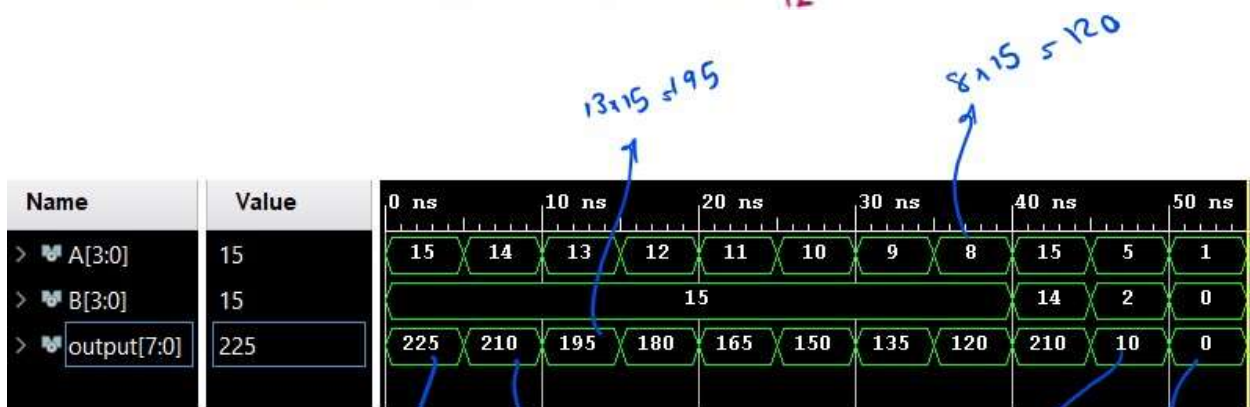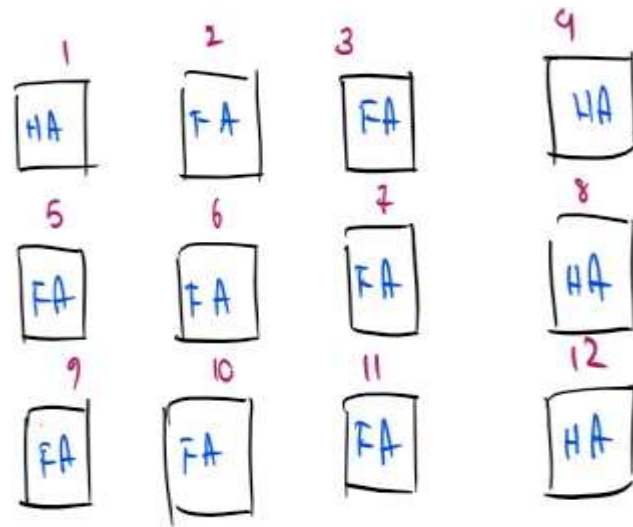

Handwritten calculations and annotations:

- $15 \times 15 = 225$
- $14 \times 15 = 210$
- $13 \times 15 = 195$
- $12 \times 15 = 180$
- $11 \times 15 = 165$
- $10 \times 15 = 150$
- $9 \times 15 = 135$
- $8 \times 15 = 120$
- $7 \times 15 = 105$
- $6 \times 15 = 90$
- $5 \times 15 = 75$
- $4 \times 15 = 60$
- $3 \times 15 = 45$
- $2 \times 15 = 30$
- $1 \times 15 = 15$
- $0 \times 15 = 0$

Array multiplier:

```

and_1_1: AND_gate port map(a => in1(0), b => in2(0), output => output_mul(0));
and_1_2: AND_gate port map(a => in1(1), b => in2(0), output => and_out(0));
and_1_3: AND_gate port map(a => in1(2), b => in2(0), output => and_out(1));
and_1_4: AND_gate port map(a => in1(3), b => in2(0), output => and_out(2));

and_1_5: AND_gate port map(a => in1(0), b => in2(1), output => and_out(4));
and_1_6: AND_gate port map(a => in1(1), b => in2(1), output => and_out(5));
and_1_7: AND_gate port map(a => in1(2), b => in2(1), output => and_out(6));
and_1_8: AND_gate port map(a => in1(3), b => in2(1), output => and_out(7));

adder_1: carry_lookahead_adder_4_bit port map
(
  A      => and_out(3 downto 0),
  B      => and_out(7 downto 4),
  Cin    => and_out(3),
  S      => adder_out(4 downto 0),
  Cout   => open
);


and_2_1: AND_gate port map(a => in1(0), b => in2(2), output => and_out(8));
and_2_2: AND_gate port map(a => in1(1), b => in2(2), output => and_out(9));
and_2_3: AND_gate port map(a => in1(2), b => in2(2), output => and_out(10));
and_2_4: AND_gate port map(a => in1(3), b => in2(2), output => and_out(11));

adder_2: carry_lookahead_adder_4_bit port map
(
  A => and_out(11 downto 8),
  B => adder_out(4 downto 1),
  Cin => and_out(3),
  S => adder_out(9 downto 5),
  Cout => open
);

and_3_1: AND_gate port map(a => in1(0), b => in2(3), output => and_out(12));
and_3_2: AND_gate port map(a => in1(1), b => in2(3), output => and_out(13));
and_3_3: AND_gate port map(a => in1(2), b => in2(3), output => and_out(14));
and_3_4: AND_gate port map(a => in1(3), b => in2(3), output => and_out(15));


adder_3: carry_lookahead_adder_4_bit port map
(
  A => and_out(15 downto 12),
  B => adder_out(9 downto 6),
  Cin => and_out(3),
  S => output_mul(7 downto 3),
  Cout => open
);

```

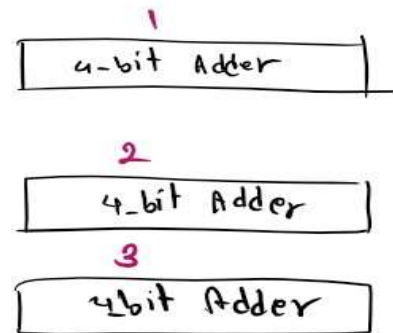

output to input

out-put to input

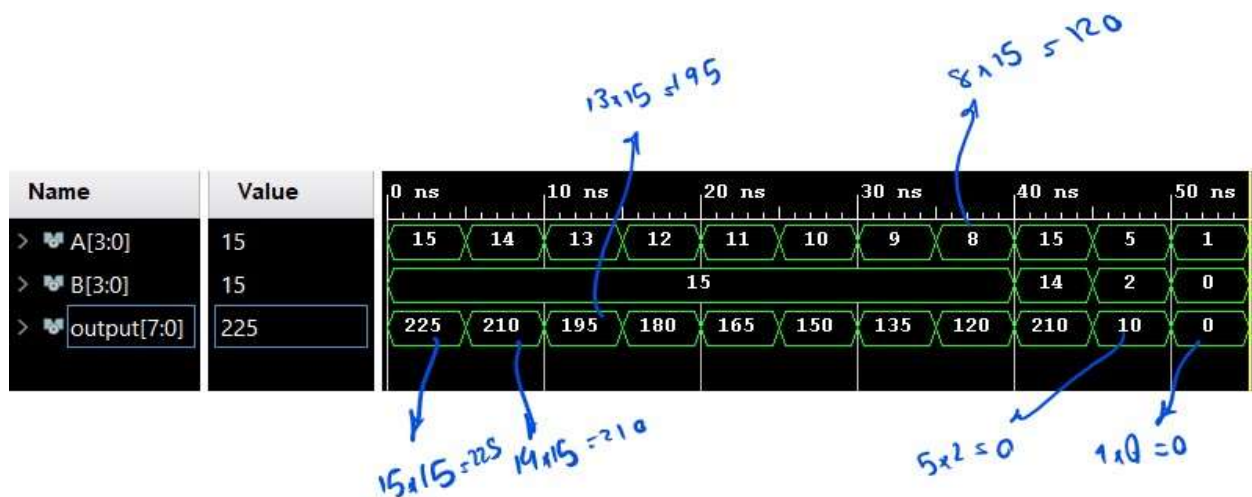

Carry save adder:

